

Birla Institute of Technology and Science – Pilani, Hyderabad Campus
Second Semester 2018-19

CS F342: Computer Architecture Assignment (20 Marks)

1. (a) Implement 4-stage pipelined processor in Verilog. This processor supports data transfer (mov), addition (add) and Unconditional Jump (J) instructions only. The processor should implement forwarding to resolve data hazards. The processor has Reset, CLK as inputs and no outputs. The processor has instruction fetch unit, register file (with 8 8-bit registers), Execution and Writeback unit. Read and write operations on Register file can happen simultaneously and should be independent of CLK. The processor also contains three pipelined registers IF/ID, ID/EX and EX/WB. When reset is activated the PC, IF/ID, ID/EX, EX/WB registers are initialized to 0, the instruction memory and registerfile get loaded by **predefined values**. When the instruction unit starts fetching the first instruction the pipeline registers contain unknown values. When the second instruction is being fetched in IF unit, the IF/ID registers will hold the instruction code for first instruction. When the third instruction is being fetched by IF unit, the IF/ID register contains the instruction code of second instruction, ID/EX register contains information related to first instruction and so on. (Assume 8-bit PC. Also Assume Address and Data size as 8-bits)
- The instruction and its **8-bit instruction format** are shown below:

mov DestinationReg, SourceReg (Moves data in register specified by register number in Rsrc field to a register specified by register number in RDst field. Opcode for mov is 00)

Opcode



Example usage: mov R2, R0 (R2 ← R0)

add DestinationReg, SourceReg (adds data in register specified by register number in Rsrc field to data in register specified by register number in RDst field. Result is stored in register specified by register number in RDst field. Opcode for add is 01)

Opcode



Example usage: add R2, R0 (R2 ← R2 + R0)

j L1 (Jumps to an address generated by adding PC+1 to the Signextended data specified in instruction field (5:0). Opcode for j is 11)

Opcode



Example usage: j L1 (Jump address is calculated using PC relative addressing)

Assume the register file contains 8 registers (R0-R7) each register can hold 8-bit data. On reset register file should get initialized such that R0 = 0, R1 = 1, R2 = 2, R3 = 3 ...etc. On reset assume that the instruction memory gets initialized with four instructions.

```
mov Rx, Ry
add Ry, Rx
add Rz, Ry
j L1
mov Rx, Rz
```

L1: add Rx, Rz

Where x, y, z are related to last 3 digits of your ID No.


If ID number: 20XXXXXXABCH, then

$$x = A \bmod 8 \ (A \% 8),$$

$$y = (B+2) \bmod 8 \ ((B+2) \% 8),$$

$$z = (C+3) \bmod 8 \ ((C+3) \% 8),$$

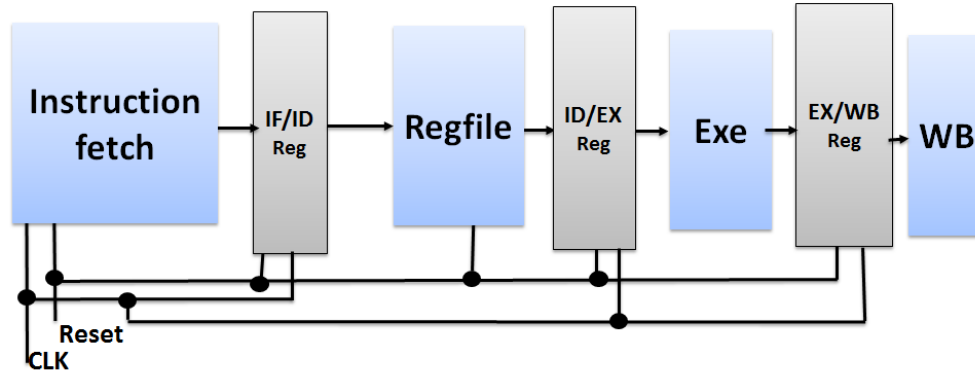A partial block level representation of 4-stage pipelined processor is shown below. **Please note that for registerfile implementation, both read and write are independent of CLK.** Write operation depends on control signal.



As part of the assignment three files should be submitted in zipped folder.

1. PDF version of this Document with all the Questions below answered with file name as IDNO_NAME.pdf.
2. Design Verilog Files for all the Sub-modules (instruction fetch, Register file, forwarding unit).
3. Design Verilog file for the main processor.

The name of the zipped folder should be in the format IDNO_NAME.zip

The due date for submission is 21-April-2019, 5:00 PM.

Name: Ayush Mall

ID No: 2016A3PS0163G

Questions Related to Assignment

1. Draw the complete Datapath and show control signals of the 4-stage pipelined processor. A sample Datapath for 5-stage pipelined MIPS processor has been discussed in class. A ppt named Assignmenthelp.ppt contains this 5-stage processor and is uploaded in CMS. You can modify this according to your specification.

The diagram illustrates the internal components and data flow of a processor. Key elements include:

- Program Counter (PC):** Receives *pc-select* and outputs *PC* to Instruction Memory.
- Instruction Memory:** Receives *PC* and outputs *Instruction* to the ALU.
- ALU:** Performs operations based on *Op* and *Op2* inputs. It outputs *Result* to the Register File.
- Register File:** Stores data in *Reg_1* and *Reg_2*. It receives *Write Data* and *Write En* signals. It outputs *Read Data* to the ALU and *Read En* to the Register File.
- Control Unit:** Receives *Control* and *Control En* signals. It outputs *Control* to the ALU and *Control En* to the Register File.
- Forwarding Unit:** Receives *Forwarding* and *Forwarding En* signals. It outputs *Forwarding* to the ALU and *Forwarding En* to the Register File.
- Exception Unit:** Receives *Exception* and *Exception En* signals. It outputs *Exception* to the ALU and *Exception En* to the Register File.

Answer:

| Instructions | Control Signals | | | | | |
|--------------|-----------------|------------|-----------|--|--|--|
| | Reg_write | Out_Select | PC_Select | | | |
| mov | 1 | 1 | 0 | | | |
| add | 1 | 0 | 0 | | | |
| j | 0 | 0 | 1 | | | |

3. Implement the Instruction Fetch block. Copy the image of Verilog code of the Instruction fetch block here

```

1
2
3  module IM_block(
4      input [7:0] PC,
5      input reset,
6      output [7:0] Instruction_code);
7      reg [7:0] Instruction_mem [31:0];
8
9      assign Instruction_code = Instruction_mem[PC];
10
11     always@(negedge reset)
12     begin
13         if(reset == 0)
14         begin
15             Instruction_mem[0] <= 8'h08;
16             Instruction_mem[1] <= 8'h41;
17             Instruction_mem[2] <= 8'h70;
18             Instruction_mem[3] <= 8'h81;
19             Instruction_mem[4] <= 8'h0E;
20             Instruction_mem[5] <= 8'h4E;
21         end
22     end
23 endmodule
24
25

```

Answer:

4. Implement the Register File and copy the image of Verilog code of Register file unit here.

```

1
2
3 module Reg_File(
4     input [2:0] Reg1,
5     input [2:0] Reg2,
6     input [2:0] Write_reg,
7     input [7:0] Data_Write,
8     input RegWr_control,
9     input reset,
10    output reg [7:0] Data_Reg1,
11    output reg [7:0] Data_Reg2
12 );
13
14    reg [7:0] Reg_mem [7:0];
15
16    always@(negedge reset)
17    begin
18        if(reset == 0)
19        begin
20            Reg_mem[0] = 0;
21            Reg_mem[1] = 1;
22            Reg_mem[2] = 2;
23            Reg_mem[3] = 3;
24            Reg_mem[4] = 4;
25            Reg_mem[5] = 5;
26            Reg_mem[6] = 6;
27            Reg_mem[7] = 7;
28        end
29    end
30
31    always@(*)
32    begin
33        Data_Reg1 <= Reg_mem[Reg1];
34        Data_Reg2 <= Reg_mem[Reg2]; //for sequential execution
35
36        if(RegWr_control == 1)
37            Reg_mem[Write_reg] <= Data_Write;
38    end
39 endmodule
40
41

```


Answer:

5. Determine the condition that can be used to detect data hazard?

Answer: $(ID_EX_Regwrite == 1) \&\&((EX_WB_Rdst == ID_EX_Rsrc) || (EX_WB_Rdst == ID_EX_Rdst))$

6. Implement the forwarding unit and copy the image of Verilog code of forwarding unit here.

Answer:

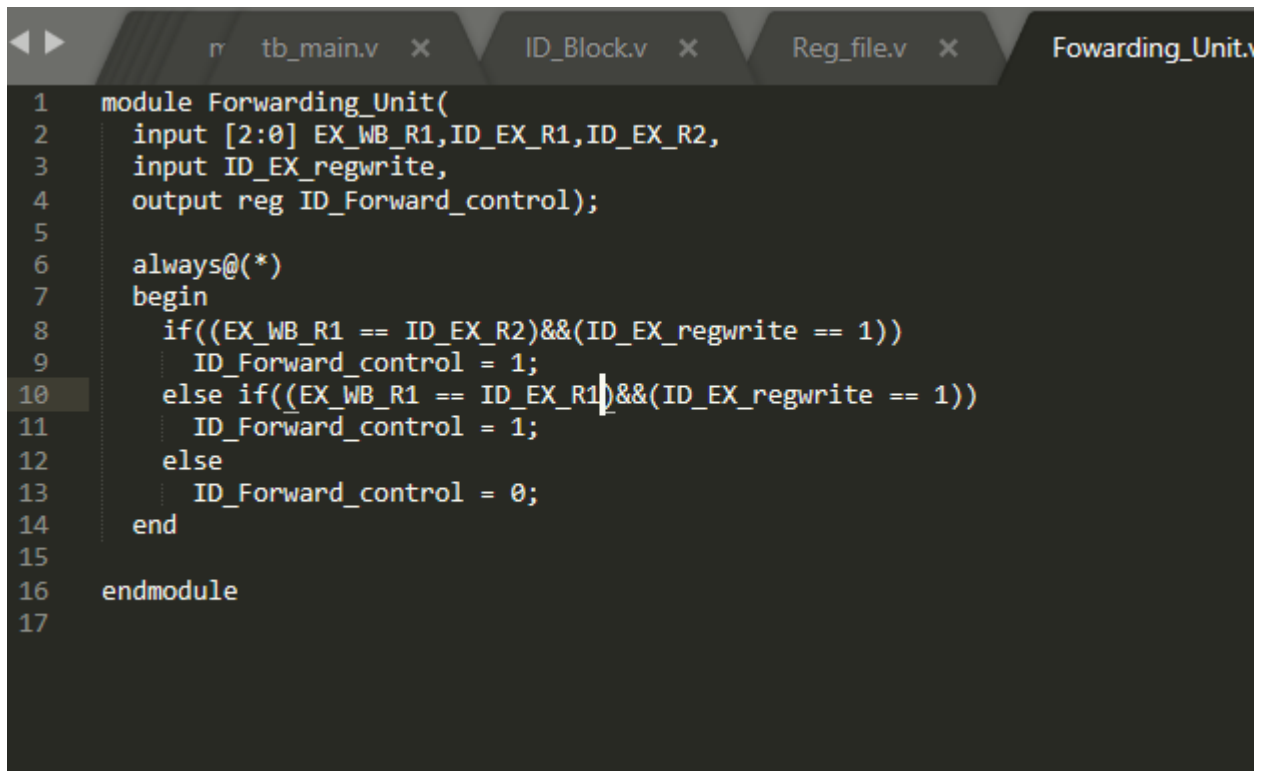A screenshot of a Verilog code editor with four tabs: 'tb_main.v', 'ID_Block.v', 'Reg_file.v', and 'Forwarding_Unit.v'. The 'Forwarding_Unit.v' tab is active, displaying the following code:

```
1 module Forwarding_Unit(  
2     input [2:0] EX_WB_R1, ID_EX_R1, ID_EX_R2,  
3     input ID_EX_regwrite,  
4     output reg ID_Forward_control);  
5  
6     always@(*)  
7     begin  
8         if((EX_WB_R1 == ID_EX_R2)&&(ID_EX_regwrite == 1))  
9             ID_Forward_control = 1;  
10        else if((EX_WB_R1 == ID_EX_R1)&&(ID_EX_regwrite == 1))  
11            ID_Forward_control = 1;  
12        else  
13            ID_Forward_control = 0;  
14        end  
15  
16    endmodule  
17
```

7. Implement complete processor in Verilog (using all the Datapath blocks). Copy the image of Verilog code of the processor here. (Use comments to describe your Verilog implementation)

```

1 module Processor(
2     input clk, reset);
3
4     |
5     wire [7:0] IF_PC_in,IF_PC_out,IF_PC_next;
6
7     wire [7:0] IF_Instruction_code;
8
9     reg [7:0] IF_ID_PC_next, IF_ID_Instruction_code;
10
11
12
13     wire [7:0] ID_Instruction_code,ID_jump_address;
14     wire [1:0] ID_Opcode;
15     wire [2:0] ID_R1,ID_R2;
16     wire [5:0] ID_address;
17     wire ID_regwrite,ID_Out_select,ID_PC_select,EX_Forward_control;
18     wire [7:0] ID_Read_data_R1,ID_Read_data_R2,ID_PC_Jump_address,ID_PC_next;
19
20     reg [7:0] ID_EX_Read_data_R1, ID_EX_Read_data_R2;
21     reg [2:0] ID_EX_R1,ID_EX_R2;
22     reg ID_EX_regwrite,ID_EX_Out_select;
23
24     wire [7:0] EX_Read_data_R1,EX_Read_data_R2,EX_added_data,EX_final_data;
25     wire [2:0] EX_R1,EX_R2;
26     wire EX_regwrite,EX_Out_select;
27
28     wire [7:0] EX_Write_data;
29
30     reg [7:0] EX_WB_Write_data;
31     reg [2:0] EX_WB_R1;
32     reg EX_WB_regwrite;
33
34     wire [2:0] WB_R1;
35     wire WB_regwrite;
36     wire [7:0] WB_Write_data;
37
38     //IF stage : Mux, PC_counter, IM
39
40     //first two letters denoting which stage that signal is coming from
41     PC_Reset PC(clk,reset,IF_PC_in,IF_PC_out);
42     MUX_21 M1(IF_PC_out,ID_PC_Jump_address,ID_PC_select,IF_PC_next);
43     Ex_block Pc_inc(1,IF_PC_next,IF_PC_in);
44     IM_block IM1(IF_PC_next,reset,IF_Instruction_code);
45

```

Answer:

```

46
47 //IF-ID Reg
48 // IF/ID Register
49 always@(posedge clk or negedge reset)
50 begin
51     if(reset == 0)
52     begin
53         IF_ID_PC_next = 0;
54         IF_ID_Instruction_code = 0;
55     end
56     else
57     begin
58         IF_ID_PC_next = IF_PC_in;
59         IF_ID_Instruction_code = IF_Instruction_code;
60     end
61 end
62
63
64
65 //ID stage : Decoder, Control Unit, Control Hazard
66 assign ID_Instruction_code = IF_ID_Instruction_code;
67 assign ID_PC_next = IF_ID_PC_next;
68
69 ID_block ID(ID_Instruction_code, ID_Opcode, ID_R1, ID_R2, ID_address);
70
71 Control_Unit CU(ID_Opcode, ID_regwrite, ID_Out_select, ID_PC_select);
72
73 Reg_File RF(ID_R1, ID_R2, WB_R1, WB_Write_data, WB_regwrite, reset, ID_Read_data_R1, ID_Read_data_R2);
74
75 Sign_Extend S1(ID_address, ID_jump_address);
76
77 Ex_block addJump(ID_PC_next, ID_jump_address, ID_PC_Jump_address);
78
79 // ID/EX Register

```

```

// ID/EX Register
always@(posedge clk or negedge reset)
begin
    if(reset == 0)
    begin
        ID_EX_R1 = 0;
        ID_EX_R2 = 0;
        ID_EX_Read_data_R1 = 0;
        ID_EX_Read_data_R2 = 0;
        ID_EX_regwrite = 0;
        ID_EX_Out_select = 0;
    end
    else
    begin
        ID_EX_R1 = ID_R1;
        ID_EX_R2 = ID_R2;
        ID_EX_Read_data_R1 = ID_Read_data_R1;
        ID_EX_Read_data_R2 = ID_Read_data_R2;
        ID_EX_regwrite = ID_regwrite;
        ID_EX_Out_select = ID_Out_select;
    end
end
end

```



```

5 //Ex_block : ALU, Forwarding unit
6
7
8 assign EX_Read_data_R1 = ID_EX_Read_data_R1;
9 assign EX_Read_data_R2 = ID_EX_Read_data_R2;
10 assign EX_regwrite = ID_EX_regwrite;
11 assign EX_Out_select = ID_EX_Out_select;
12 assign EX_R1 = ID_EX_R1;
13 assign EX_R2 = ID_EX_R2;
14
15
16 Forwarding_Unit FU(EX_WB_R1,ID_EX_R1,ID_EX_R2,ID_EX_regwrite,EX_Forward_control);
17
18 MUX_21 muxFWD(EX_Read_data_R1,WB_Write_data,EX_Forward_control,EX_final_data);
19
20 Ex_block EX(EX_final_data,EX_Read_data_R2,EX_Added_data);
21
22 MUX_21 mux2(EX_added_data,EX_Read_data_R2,EX_Out_select,EX_Write_data);
23
24
25
26 // EX/WB Register
27 always@(posedge clk or negedge reset)
28 begin
29     if(reset == 0)
30     begin
31         EX_WB_Write_data = 0;
32         EX_WB_regwrite = 0;
33         EX_WB_R1 = 0;
34     end
35     else
36     begin
37         EX_WB_Write_data = EX_Write_data;
38         EX_WB_regwrite = EX_regwrite;
39         EX_WB_R1 = EX_R1;
40     end
41 end
42
43 // WB Stage
44 assign WB_Write_data = EX_WB_Write_data;
45 assign WB_regwrite = EX_WB_regwrite;
46 assign WB_R1 = EX_WB_R1;
47
48
49
50
51
52 endmodule

```

8. Test the processor design by generating the appropriate clock and reset. Copy the image of your testbench code here.

```


1  module testb_main;
2      reg clk,reset;
3
4      Processor main(clk,reset);
5
6      initial begin
7          clk = 1'b0;
8          repeat(100)
9              #10 clk = ~clk;
10             #10 $finish;
11         end
12
13         initial begin
14             reset = 1'b1;
15             #5 reset = 1'b0;
16             #10 reset = 1'b1;
17         end
18
19     endmodule
20
21

```

Answer:

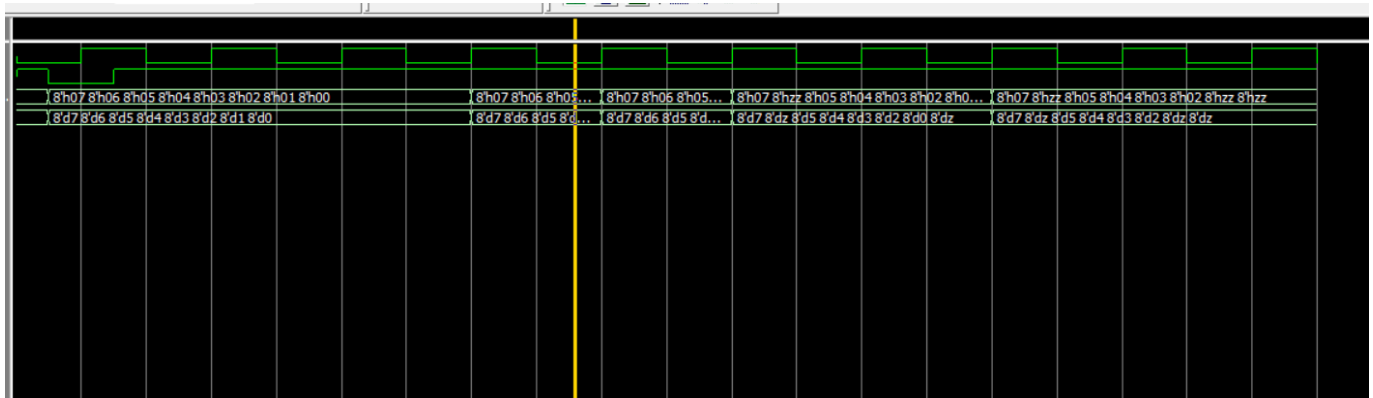9. Verify if the register file is getting updated according to the set of instructions (mentioned earlier).

Copy verified **Register file** waveform here (show only the Registers that get updated, CLK, and RESET):



Unrelated Questions

What were the problems you faced during the implementation of the processor?

Answer: For some reason, the R0 register would always take a high impedance value and any operation with it would give the value ZZ . The jump is happening.

Did you implement the processor on your own? If you took help from someone whose help did you take? Which part of the design did you take help for?

Answer: I implemented it on my own. I had my confusions as to how to solve the control hazard. I took help from Kushagra Shah in preventing control hazard. He also suggested that I should declare all my registers in the main processor file itself, which I did.

Honor Code Declaration by student:

- My answers to the above questions are my own work.
- I have not shared the codes/answers written by me with any other students. (I might have helped clear doubts of other students).
- I have not copied other's code/answers to improve my results. (I might have got some doubts cleared from other students).

Name: Ayush Mall
ID No.: 2016a3ps0163G

Date: 2016A3PS0163g